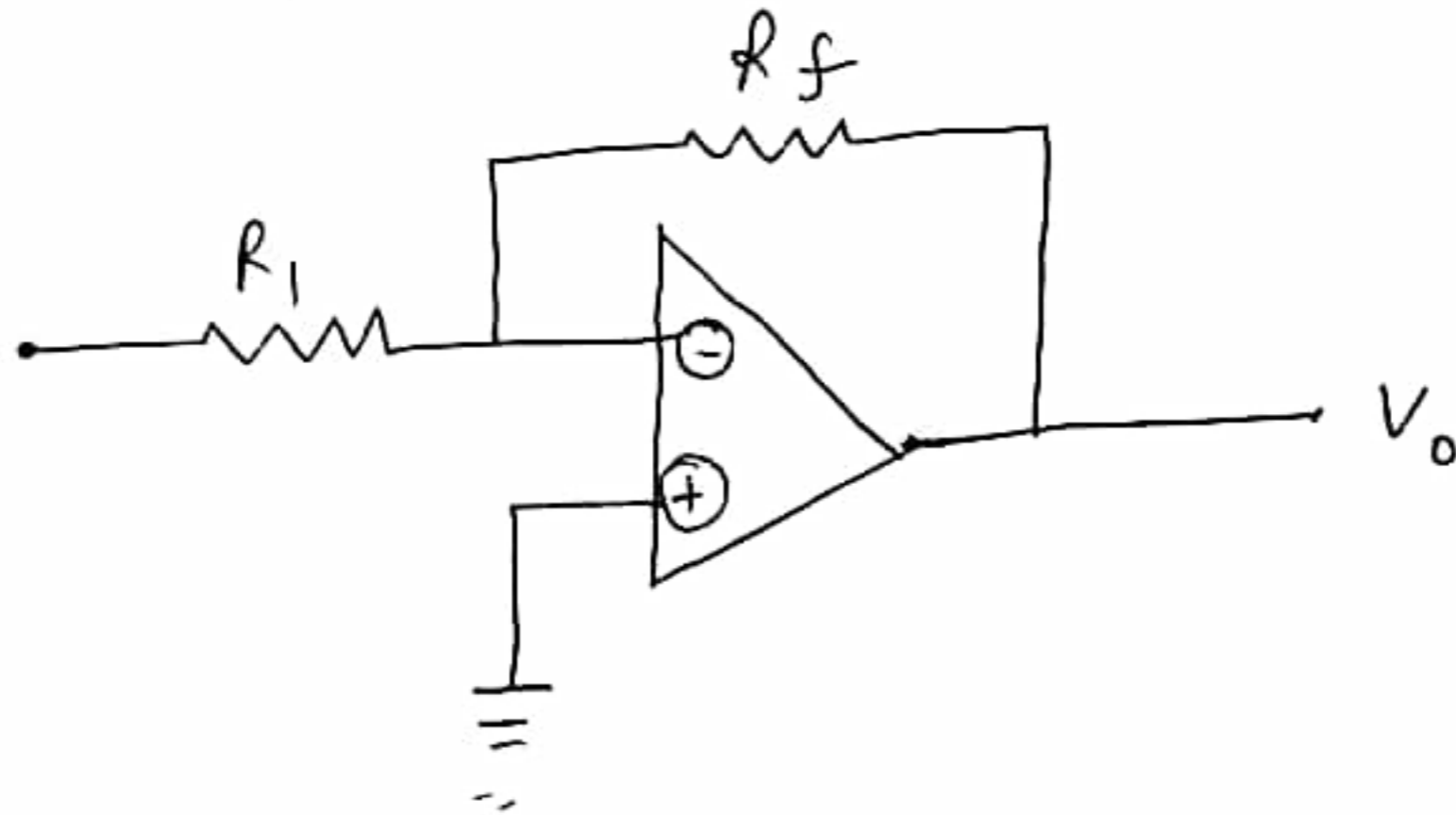


- Operational Amplifier
 - Basic op-Amp (Operation of OP-AMP as a constant gain multiplier)
 - Applications of op-AMP
- Numericals related to op-Amp


Basic OP-AMP (Operation of OP-AMP as a constant gain multiplier)



Voltage gain $\left(\frac{V_o}{V_i} \right) = - \frac{R_f}{R_1}$

Virtual ground :-

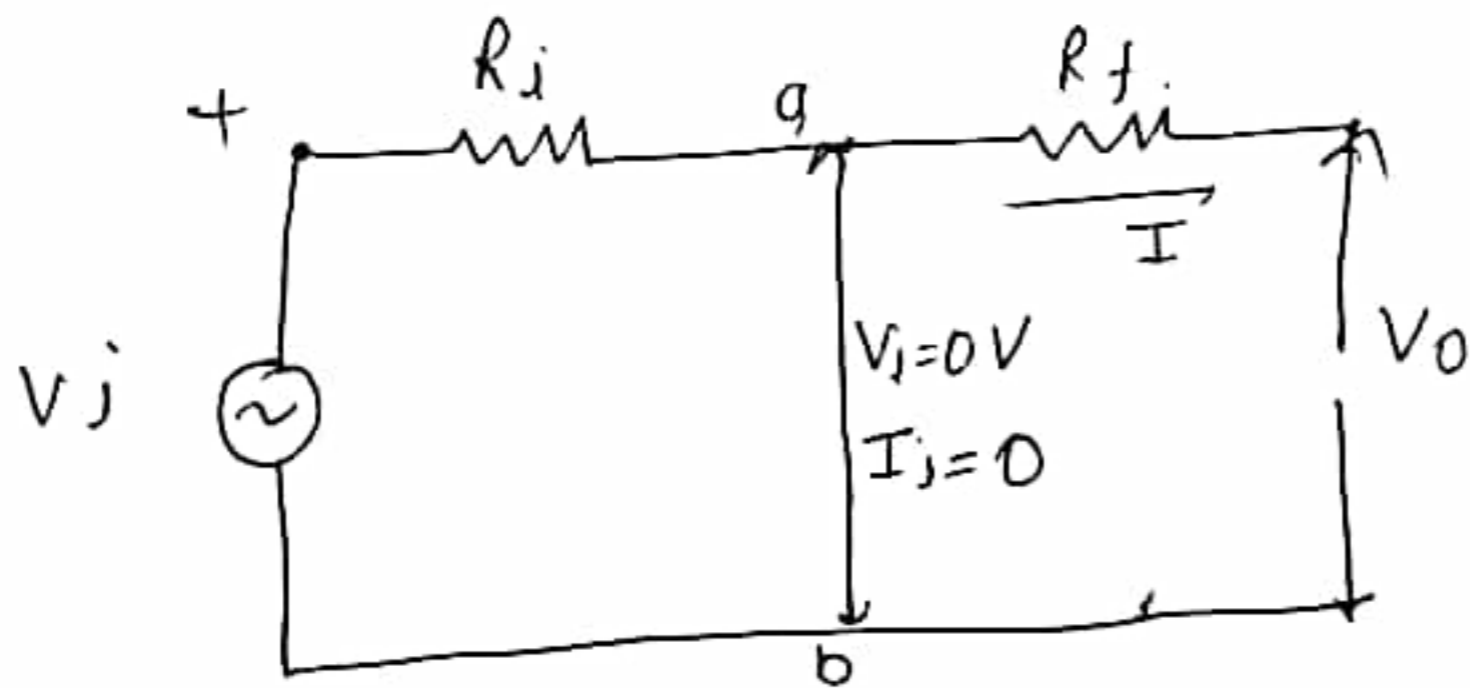The concept of virtual ground implies that although the input voltage is about 0V, there is no current through the input of the amplifier to the ground.



The line across a and b indicates that a short exist $V_i = 0V$. But the virtual short is that no current passes through the short to the ground.


$$\therefore \boxed{\frac{V_o}{V_i} = -\frac{R_f}{R_i}}$$

* The concept of virtual ground helps us to determine the overall voltage gain in a simple manner.

Applications of OP-AMP

- ① Adder or Summing Amplifier.
- ② OP-AMP Subtractor
- ③ Inverting Amplifier
- ④ Non-inverting amplifier
- ⑤ OP-AMP Integrator
- ⑥ OP-AMP Differentiator.

④ Adder or Summing Amplifier.

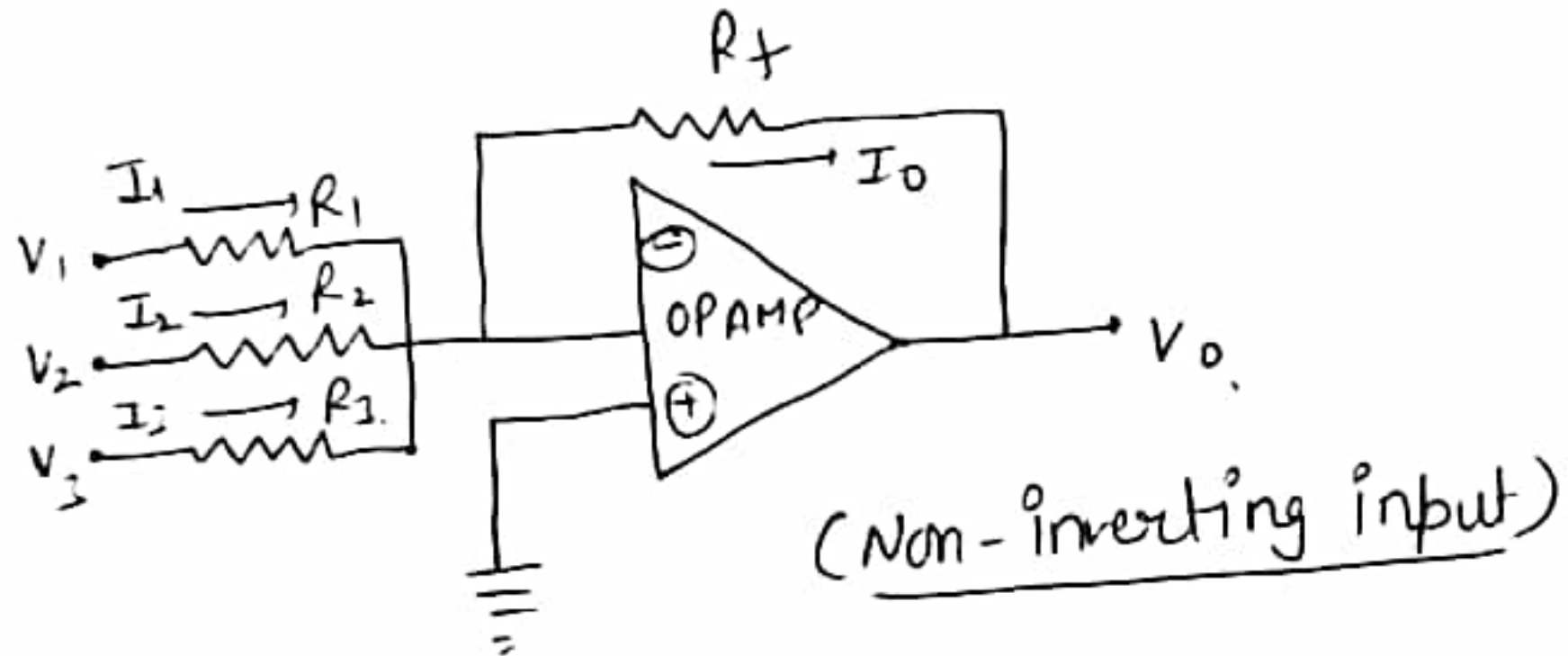

According to Kirchhoff's Current law.

$$I_1 + I_2 + I_3 = I_0$$

$$\text{or } \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = \frac{-V_0}{R_f}$$

$$V_0 = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

If $R_1 = R_2 = R_3 = R$,

then $V_0 = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$


$$= -\frac{R_f}{R} (V_1 + V_2 + V_3)$$

If $R_f = R$

$$V_0 = -(V_1 + V_2 + V_3)$$

* Negative sign shows that the output voltage is out of phase with the sum of input voltages.

② OP-AMP Subtractor

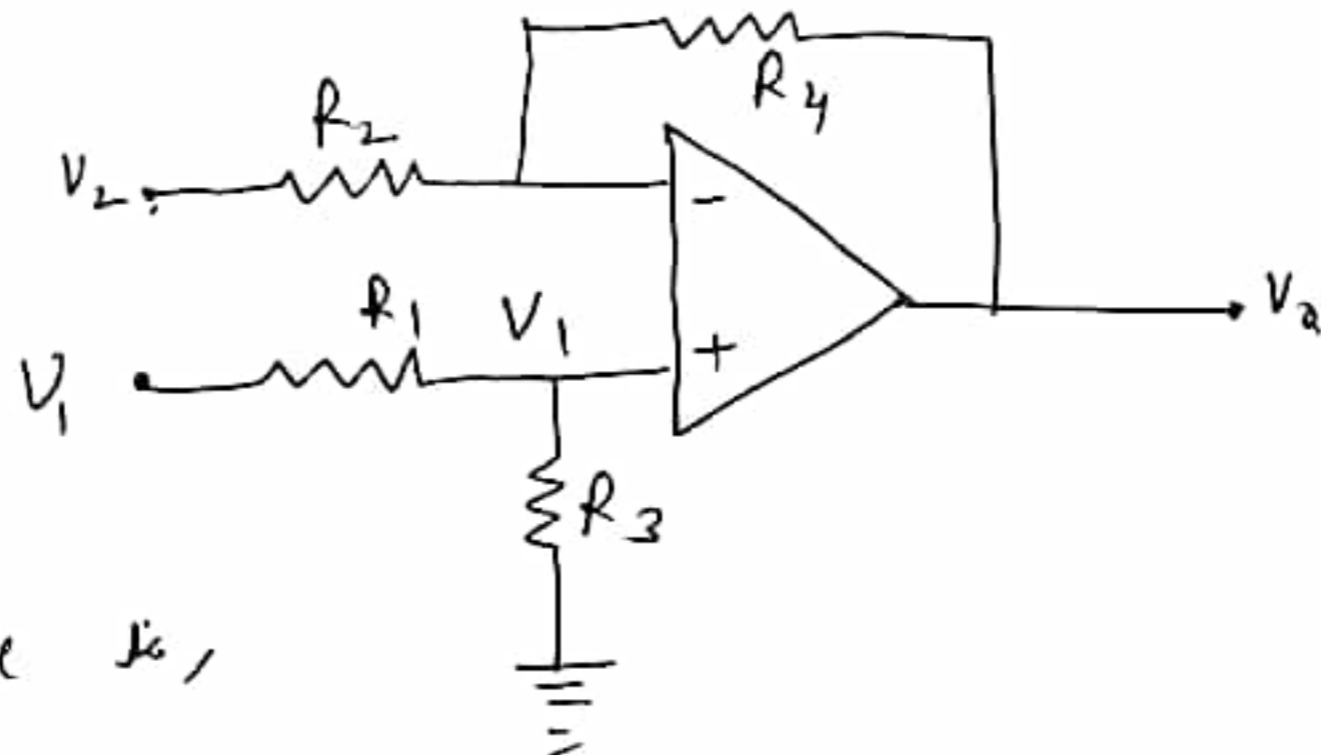


Output voltage is,

$$V_0 = \left(\frac{R_3}{R_1 + R_2} \right) \left(\frac{R_2 + R_4}{R_2} \right) V_1 - \frac{R_4}{R_2} V_2$$

if $R_1 = R_2 = R_3 = R_4 = R$

$$V_0 = \left(\frac{R}{R} \right) \left(\frac{R+R}{R} \right) V_1 - \frac{R}{R} V_2 \Rightarrow \boxed{V_0 = V_1 - V_2}$$

③ Inverting Amplifier.

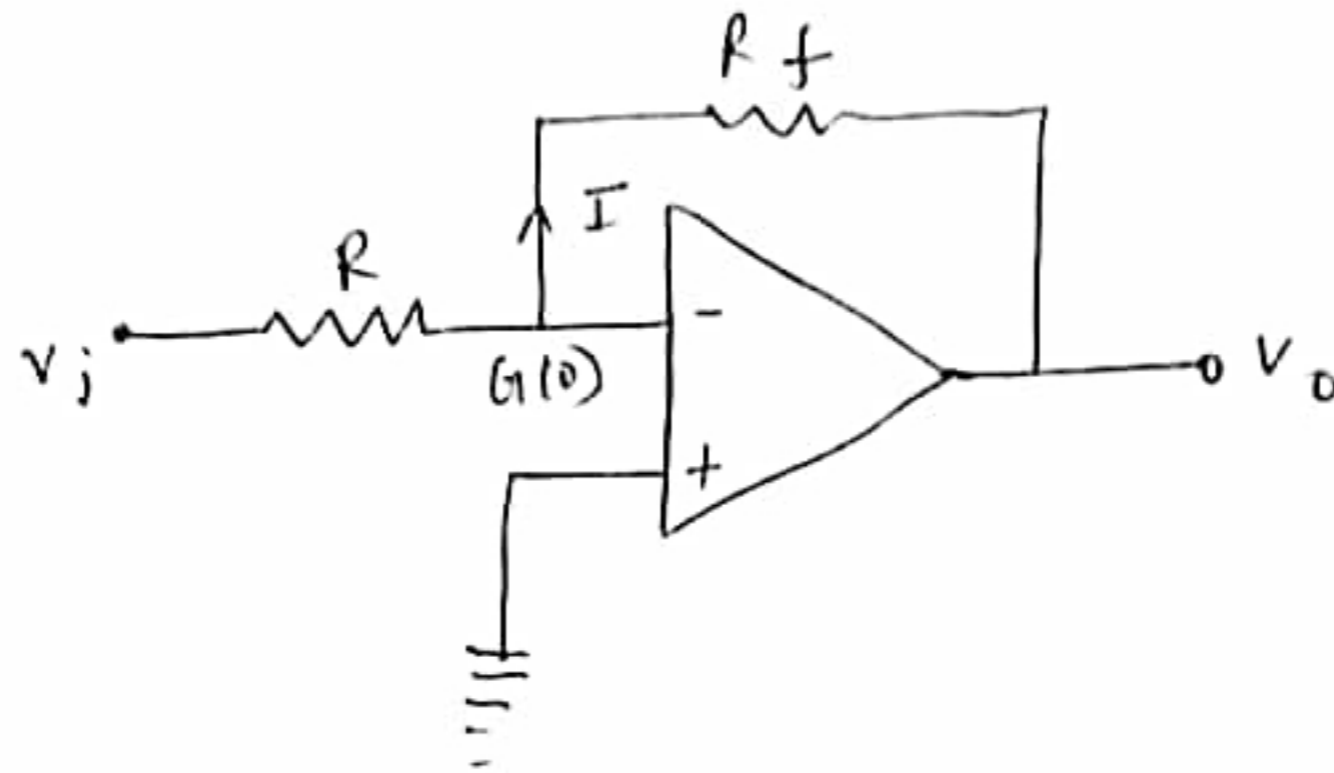

Since point G_1 is practically grounded,
so potential at $G_1 = 0$

$$I = \frac{V_i - 0}{R} = \frac{V_i}{R}$$

Acc. to Kirchoff's Current Law

$$\frac{V_i}{R} = \frac{0 - V_o}{R_f}$$

$$\frac{V_i}{R} = -\frac{V_o}{R_f}$$

$$\boxed{\frac{V_o}{V_i} = -\frac{R_f}{R}}$$

$\frac{V_o}{V_i} = A_v =$ Voltage gain of the amplifier

So, $\boxed{A_v = -\frac{R_f}{R}}$

-ve sign shows \rightarrow Phase difference between output voltage & input voltage is 180° .
 output voltage - inverted w.r.t. to input voltage. Thank You